Intelligent Humidistat



Submitted by: Group 67

Siddhant Singh Vattsa 2020A3PS1832G

Suchetan R S 2020A3PS1760G

Chetan Ghodke 2020A3PS1495G

Visisht Bhardwaj 2020A3PS1757G

Sakshi Gupta 2020A8PS2036G

Puneet Tyagi 2020AAPS1598G

Table of Contents

- 1. Design Problem
- 2. Design Specifications
- 3. Assumptions
- 4. Hardware Requirements
 - 4.1. ADC Specifications
- 5. Sensor Specifications
 - 5.1. Temperature Sensor WE700
 - 5.2. Humidity Sensor HIH 4030/31 series
 - 5.3. LM016L Hitachi LCD module with an inbuilt controller LSI HD44780
- 6. Memory Interfacing
- 7. I/O Interfacing (8255(H), 8255(T), 8253, 8259)
- 8. Design Components
 - 8.1. Connections to 8086 (Microprocessor)
 - 8.2. Connections to 8284 (Clock Generator)
 - 8.3. Connections to 74LS373 Octal Latches
 - 8.4. Connections to 74LS245 Octal Buffers
 - 8.5. Interfacing of ADC(H)with 8255(H)
 - 8.6. Interfacing of 8259 with 8253
 - 8.7. Interfacing of ADC(T)with 8255(T)
 - 8.8. Interfacing of 8253 with ADC0808(T) and ADC0808(H)
 - 8.9. Connections to Temperature sensor WE700 and Humidity sensor HIH4030
 - 8.10. Interfacing of LCD with 8255(H) and 8255 (T)
 - 8.11. Simple Relay Interfaced with RELAYH (PC6) from 8255 (T)
- 9. Software Flowchart

User Requirements

P 23: System to be designed – Intelligent Humidistat

System Description: A humidistat is supposed to be reset according to the outside temperature — as the outside temperature falls the humidity level inside the house should be set lower. The purpose of this project is to develop a humidistat which senses the outside temperature and adjusts the humidity accordingly. Two sensors are required: outside temperature and inside humidity. Output is provided via a simple relay with the humidifier (presumably on the furnace) being on or off. Also readings from the humidity and temperature sensors must be displayed on LCD display. The entire system can be turned on or off using a single switch.

Technical Specifications:

- 1. Measurement of external Temperature in and % internal relative humidity.
- 2. Design suited to a room of approximate dimensions of 9 X 7 X 4.5 (L X B X H in meters).
- 3. Adjusting of the humidity in the room based on the external temperature; this is done with the help of a humidifier.
- 4. The output to switch on/off the humidifier is given via a simple relay to indicate the state (on/off) of the humidifier.
- 5. Displaying the temperature (in °C) and relative humidity (in %) on the LCD every 1 minute.
- 6. The resolution of the temperature sensor WE700 is 1 °C.
- 7. Range of the temperature sensor $(-50^{\circ}\text{C} 50^{\circ}\text{C})$

Assumptions:

- 1) The temperature outside ranges from 0°C to 50°C and the relative humidity inside the room ranges from 25 % to 55 %.
- 2) We find the temperature and the average humidity of the room via the help of a number of sensors.
- 3) The temperature sensors is located as follows:
 - One on the outer wall.
- 4) The humidity sensors are located as follows:
 - One on each corner of the ceiling. (4 sensors)
- 5) Chart for optimal humidity ranges at given temperature range

Temperature (in deg C)	Relative
	Humidity
0-5	27%-30%
5-10	30%-33%
10-15	33%-35%
15-20	35%-38%
20-25	38%-40%
25-30	40%-43%
30-35	43%-45%
35-45	45%-48%
45-50	48%-50%

Components used with justification

wherever required

- 1. Microprocessor 8086
- 2. Octal 8-bit buffer -74LS245 (x2) [to separate data bus]
- 3. Octal 8-bit latch 74LS373(x3) [to separate address bus]
- 4. Temperature Sensors WE700 (x1)

[High Quality, rugged instrument, precision RTD, wall mountable, temperature range which suits our design]

5. Humidity Sensors – HIH4030 (x7)

[Very accurate, low response time, stable, cost effective, resistant to dust and other chemicals]

- 6. Humidifier (x1) [controls inside relative humidity]
- 7. LCD LM016L (x1) [Displays outside temperature and inside RH]
- Programmable Peripheral Interface 8255(x2)
 [Interfaces ADC & LCD]
- 9. Decoder- 74LS138(x2) [Memory, I/O Addressing]
- 10. Programmable Interval Timer 8253(x1) [provides clock to ADC]
- 11. Programmable Interrupt Controller 8259(x1) [raises an interrupt to 8086 every one minute]
- 12. 74LS32 IC containing 4 OR gates. (x1)
- 13. NOT ICs 7404 (x4)
- 14. ROM chips (4K each) 2732 (x4)

[ROM required at reset address FFFF0h and at 00000h (IVT location)]

15. RAM chips (2K each) — 6116 (x2)

[For stack and temporary storage of data]

- 16. Simple Relay(x1) [Controls switching ON/OFF the humidifier]
- 17. Clock Generator 8284 (x1) [Provide clock to 8086]
- 18. Analog to Digital Convertor 0808 (x2)

[Converts analog inputs from sensors to digital values]

ADC Specifications:

- 1) No of analog inputs = 8
- 2) No of ADCs used = 2
- 3) Size of ADC = 8 bit
- 4) Resolution of ADC = 5 V / 256 = 19.532 mV

Sensor specifications

• Temperature Sensor WE700:



WE700 – Analog Temperature sensors

Output = 4 to 20 mA

Operating voltage = $10-36 V_{DC}$

Range = -50°C to 50°C

Accuracy: ±0.1°C

Current drawn : same as sensor output

Warm up time = 3 secs

• Humidity Sensor HIH 4030/31 series:



HIH-4030/31 Series (Honeywell) including a SMD (surface mount device)

Accuracy = ± 3.5 % RH

Response time = 5 s (average)

Settling time = 70 ms (max)

Input Voltage supply = 4 - 5.8 V (DC)

Input Current supply = $0 - 500 \mu A$

%RH value for a given value of V_{out} =

$$\frac{Vout-Zero\ offset}{Slope} = \frac{Vout-0.9}{58}$$

$$0.0307$$

Operating humidity: 0-

100% RH Operating

temperature: -40 to 85 °C

Output voltage at assumed range (25-55 %) = 1.725 - 2.645V

LM016L Hitachi LCD module with an inbuilt controller LSI HD44780:



Display: 16 characters * 2 lines

Power Supply for LCD drive: 0 - 6.5V

Operating Temperature: 0 - 50 °C

Power supply current ($V_{DD} = 5 \text{ V}$): 1 - 3 mA

Memory Interfacing

• ADDRESSING:


ROM $1 - 8k: 00000_H - 01FFF_H$


ROM 2 - 8k: 02000_H - 03FFF_H

RAM $1 - 4k: 04000_H - 04FFF_H$

ROM 3 – 8k: FE000_H – FFFFF_H

• DECODING LOGIC:

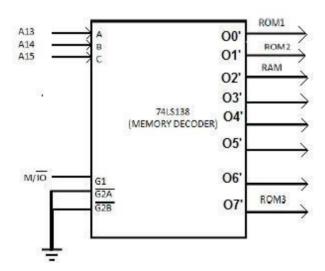

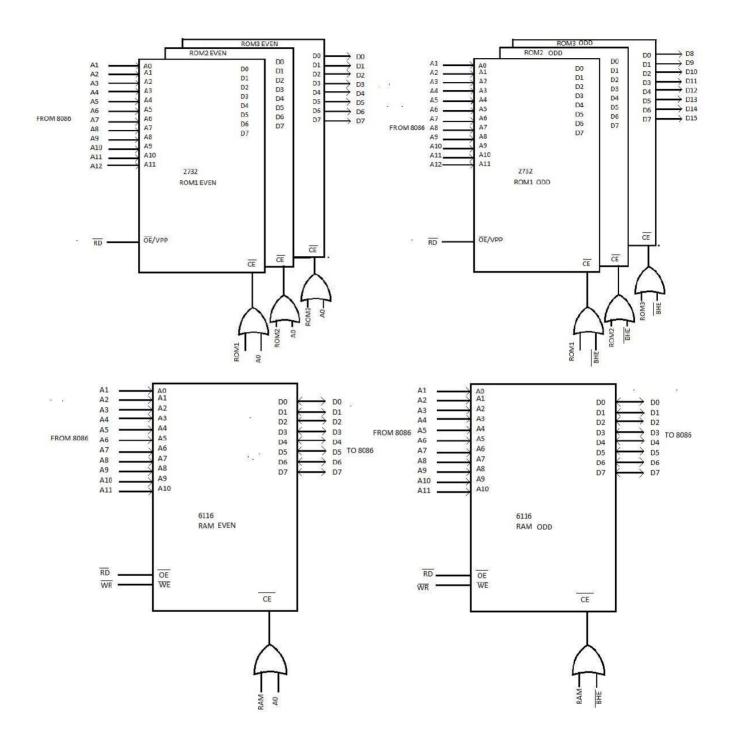

I/O Interfacing (8255(H), 8255(T), 8253)

• ADDRESSING:


 $8255(H): 00_{H} - 06_{H}$

 $8255(T): 08_H - 0E_H$

8253: 10_H - 16_H


8259: 18_H - 1A_H

• DECODING LOGIC:

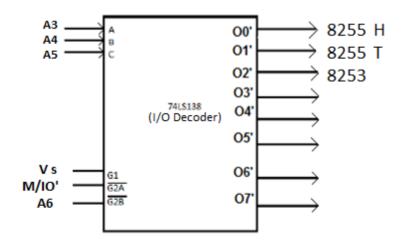


Design Components


• Connections to 8086 microprocessor

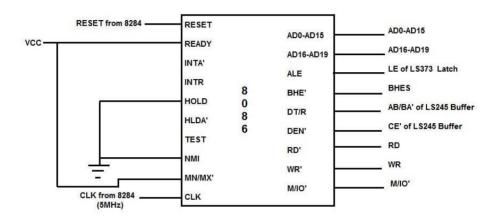



• Connections to 8284 Clock generator

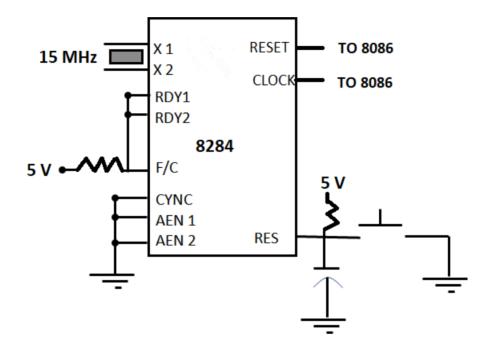


• Connections to 74LS373 Octal Latches

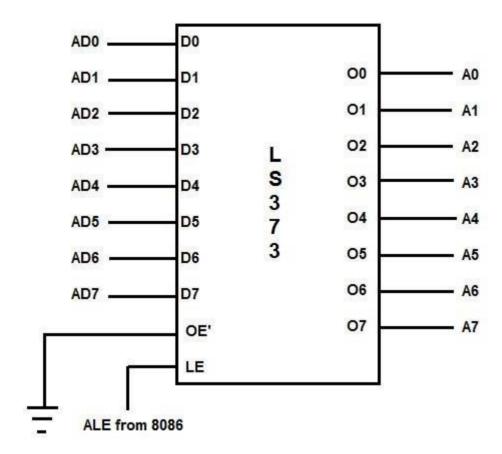

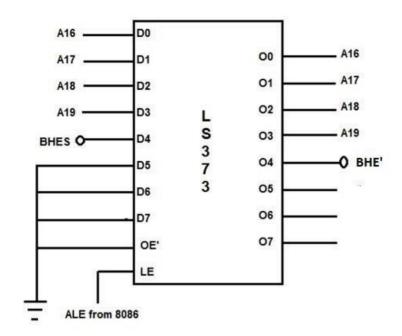


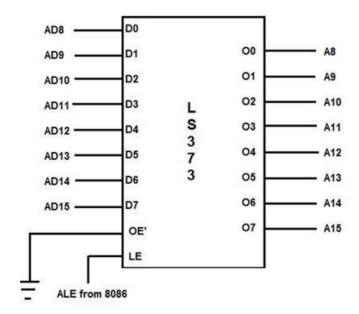

• Connections to 74LS245 Octal Buffers

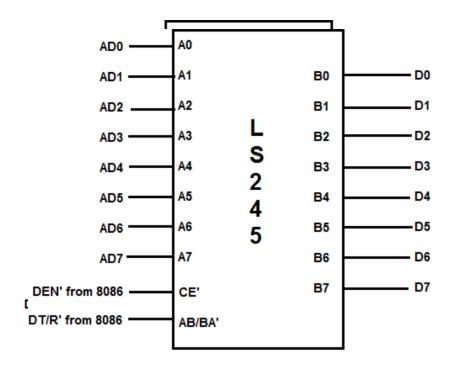


• Interfacing of ADC(H) with 8255(H)

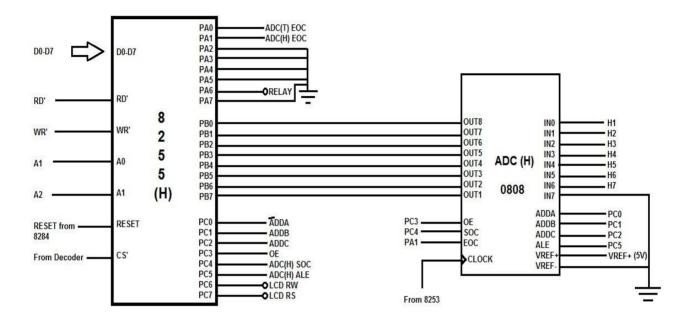


• Interfacing of 8259 with 8253

			1	A
$\overline{\text{CS}} \rightarrow$	1	28	(Vcc
$\overline{WR} \rightarrow$	2	27	-	A_0
$\overline{\text{RD}} \rightarrow$	3	26		INTA
$D_7 \leftrightarrow$	4	25	-	IR ₇
$D_6 \leftrightarrow$	5	24	-	IR_6
$D_5 \leftrightarrow$	6	23	(IR_5
$D_4 \leftrightarrow$	7	22	(IR_4
$D_3 \leftrightarrow$	8	21	\leftarrow	IR_3
$D_2 \leftrightarrow$	9	20	(IR ₂
$D_1 \leftrightarrow$	10	19	(IR ₁
$D_0 \leftrightarrow$	11	18	(IR_0
$CAS_0 \leftrightarrow$	12	17	->	INT
$CAS_1 \leftrightarrow$	13	16	\leftrightarrow	SP/EN
$Gnd \rightarrow$	14	15	\leftrightarrow	CAS ₂


• Interfacing of ADC(T) with 8255(T)

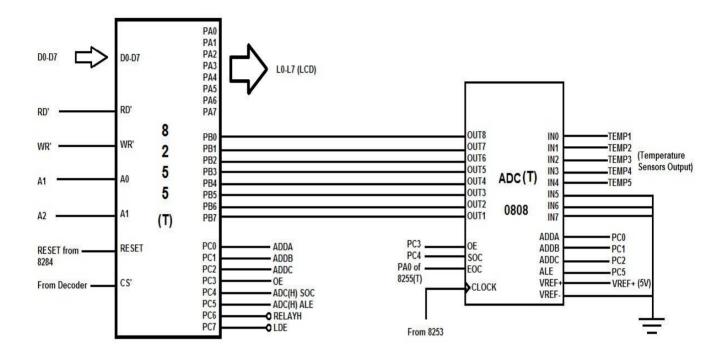


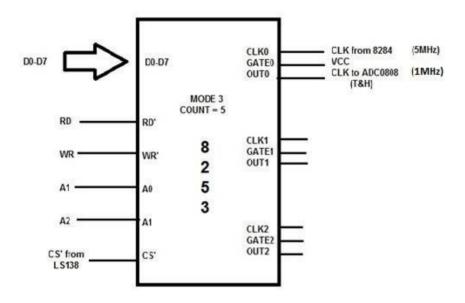• Interfacing of 8253 with ADC0808(T) and ADC0808(H)




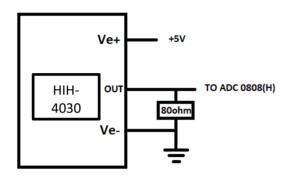Connections to Temperature sensor LMT85 and Humidity sensor HIH4030




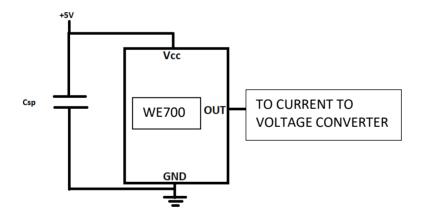

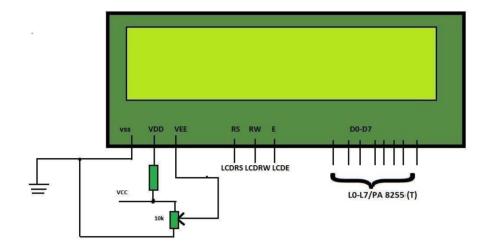• Interfacing of LCD with 8255(H) and 8255 (T)



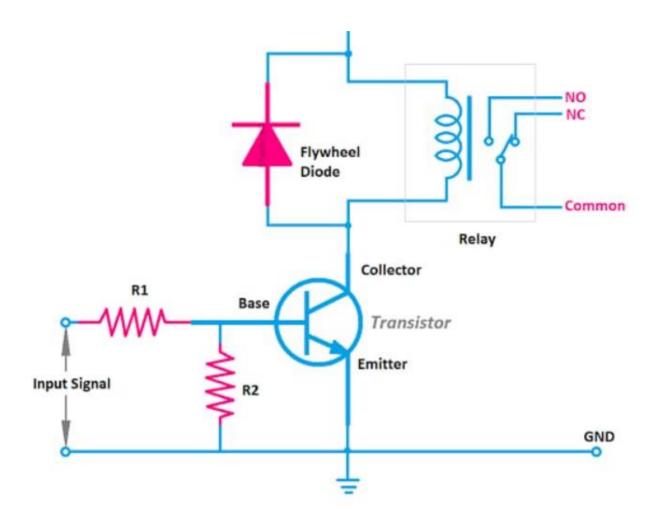• Simple Relay Interfaced with RELAYH(PC6) from 8255 (T)



Software Flowchart

